

Digital ASIC Design : Midterm Exam

Name: Skanda Krishnan Balasubramanian


Designing a Simplified version of Google's Tensor Processing Unit.

Abstract

The project described below is a simplified version of Googles Tensor Processing Unit. The goal of this project is to design this unit using sub units such as the multiply and accumulate, quantization and activation units. After which iverilog and Cadence Virtuoso is used to functionally verify the design.

 Question 1 : Designing the MAC Unit

The block diagram of the MAC unit is given below:



There are mainly 2 input Data and 3 output Data: The input data is the Ain and Win and the output is the Aout, Wout and the Pout. The Aout is passed to the next MAC in the same row while Wout and Pout are passed to the next MAC in the same column. Additional data valid signal are also given to maintain the context of the incoming and outgoing data. Pin and Pout are 24 bits wide while Ain,Aout,Win and Wout are 8 bits wide

```
always @(posedge clk or posedge rst) begin
    if(rst) begin
        aout <= 8'd0;
        dv_aout <= 1'b0;
    end
    else if(dv_ain)begin
        aout <= ain;
        dv_aout <= 1'b1;
    end
    else begin
        aout <= 8'd0;
        dv_aout <= 1'b0;
    end
end
```

flipflop defining aout

```
always @(posedge clk or posedge rst) begin
    if(rst)begin
        wout <= 8'd0;
        dv_wout <= 1'b0;
    end
    else if(init_win)begin
        wout <= win;
        dv_wout <= dv_win;
    end
end
```

flipflop defining wout

```
always @(posedge clk or posedge rst)begin
    // if(dv_aout && dv_wout && dv_pin)begin
    // if(dv_aout && dv_wout)begin
    pout <= {8'd0,prod} + pin;
    dv_pout <= 1'b1;
    end
    else begin
        pout <= 24'd0;
        dv_pout <= 1'b0;
    end
end
```



flipflop defining pout

Iverilog testing:

```
skanda@LAPTOP-3RMLJVKC:~/asic_design/midterm$ iverilog tb_mac.v mac.v
skanda@LAPTOP-3RMLJVKC:~/asic_design/midterm$ vvp a.out
1000
win = 3
ain = 2
pin = 2
pout = (w*a)+p = 8
VCD info: dumpfile wave_mac.vcd opened for output.
skanda@LAPTOP-3RMLJVKC:~/asic_design/midterm$
```

$$pout = (3*2) + 2 = 8$$

Cadence Waveform:

 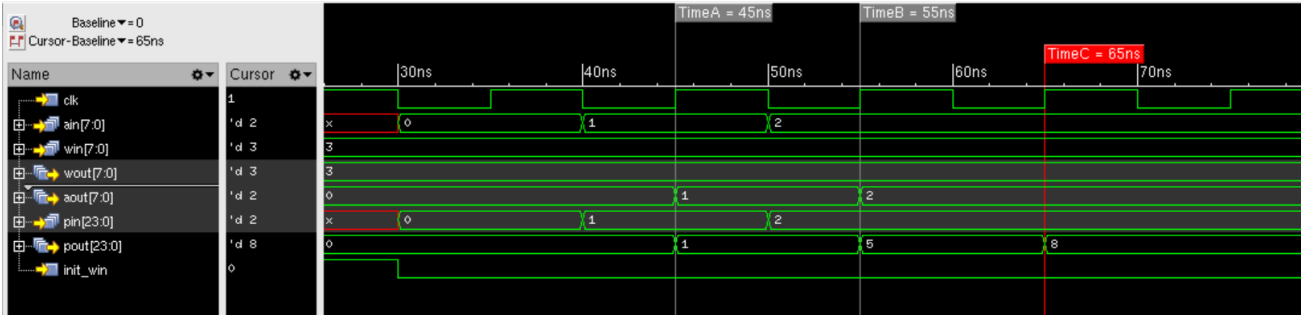

Question 2: Quantization Unit

The quantization unit is defined as an upper bounding unit where in the products are upper bounded from 24 bits to 8 bits. The way we do this if the 24 bit product is greater than 255 then the output of the quantization unit is 255. If it is less than 255 then the output will be the value itself. The quantization unit described below is handling 4 24 bit inputs and giving 4 8-bit outputs after quantization. No clock is used and computation is done combinatorially. Additional data valid pins are used to maintain the context and validity of data.

```

genvar i;
generate
  for(i = 0; i < 4; i = i + 1) begin
    always @(*) begin
      if (rst) begin
        qout[(i*8)+7:(i*8)] <= 8'd0;
        dv_qout[i] <= 1'b0;
      end
      else if (dv_pin[i]) begin
        if (pin[(i*24)+23:(i*24)] <= 24'd255)
          qout[(i*8)+7:(i*8)] <= pin[(i*24)+7:(i*24)];
        else
          qout[(i*8)+7:(i*8)] <= 8'd255;
          dv_qout[i] <= dv_pin[i];
        end
      else begin
        qout[(i*8)+7:(i*8)] <= 8'd0;
        dv_qout[i] <= 1'b0;
      end
    end
  end
end

```

Iverilog Test :


```

skanda@LAPTOP-3RMLJVKC:~/asic_design/ midterm$ iverilog tb_quant.v quant.v
skanda@LAPTOP-3RMLJVKC:~/asic_design/ midterm$ vvp a.out
VCD info: dumpfile wave_quant.vcd opened for output.
65
pin0 = 30, qout0 = 30
pin1 = 30, qout1 = 30
pin2 = 30, qout2 = 30
pin3 = 30, qout3 = 30
85
pin0 = 300, qout0 = 255
pin1 = 300, qout1 = 255
pin2 = 300, qout2 = 255
pin3 = 300, qout3 = 255
105
pin0 = 100, qout0 = 100
pin1 = 200, qout1 = 200
pin2 = 300, qout2 = 255
pin3 = 400, qout3 = 255


```

anything above 255 is locked to 255.

Cadence Test and Waveform

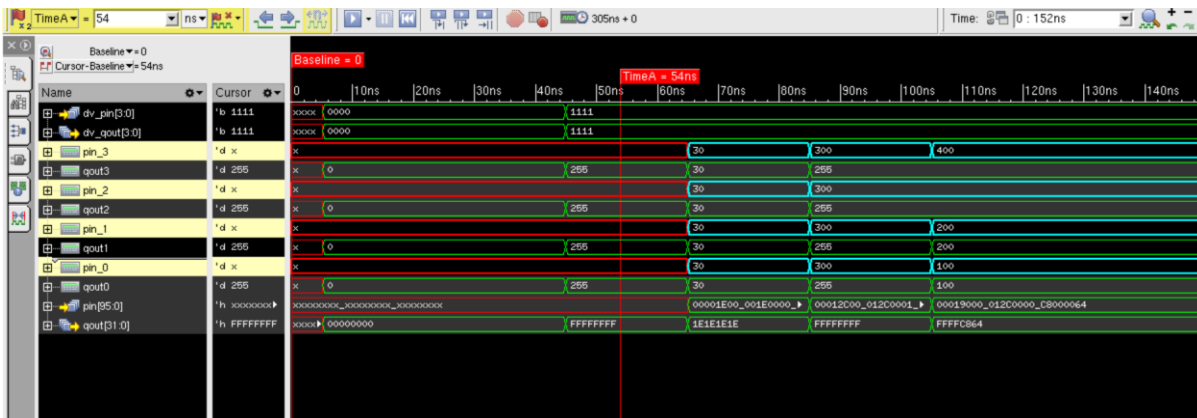

Blue traces are the inputs and the green traces are the outputs.

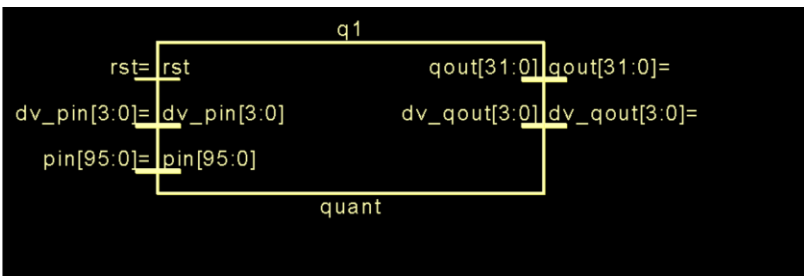

Question 2: Activation Unit

The quantization unit is defined as a lower bounding unit where in the quantized outputs are lower bounded decimal value 10. That is, if the input data is less than 10 then the output of the activation unit would be 0. If the input is greater than 10 then the output would be the same as the input. The activation unit described below is handling 4 8 bit inputs and slotting them into 127 bit bus according to the data valid. An additional state machine is inside the activation unit to slot the output products into the correct address of the feature memory.

```

genvar l;
generate
  for(l=0;l<4;l=l+1)begin
    always @(*)begin
      if(acin [(l*8)+7:l*8] > 8'd10)
        actdata [(l*8)+7:l*8] <= acin [(l*8)+7:l*8];
      else
        actdata [(l*8)+7:l*8] <= 8'd0;
      end
    end
  end
endgenerate

```

Iverilog Test :



```

skanda@LAPTOP-3RMLJWNC:~/asic_design/midterm$ iverilog tb_activ.v activ.v
skanda@LAPTOP-3RMLJWNC:~/asic_design/midterm$ vvp a.out
VCD info: dumpfile wave_activ.vcd opened for output.
65
data_valid = 1111
acin0 = 11, acout0 = 11
acin1 = 9, acout1 = 0
acin2 = 9, acout2 = 0
acin3 = 11, acout3 = 11
85
data_valid = 1111
acin0 = 9, acout0 = 0
acin1 = 11, acout1 = 11
acin2 = 11, acout2 = 11
acin3 = 9, acout3 = 0
105
data_valid = 1111
acin0 = 1, acout0 = 0
acin1 = 100, acout1 = 100
acin2 = 1, acout2 = 0
acin3 = 100, acout3 = 100
125
data_valid = 1111
acin0 = 11, acout0 = 11
acin1 = 11, acout1 = 11
acin2 = 11, acout2 = 11
acin3 = 11, acout3 = 11
145

```

anything below 10 is locked to 0.


Cadence Test and Waveform

 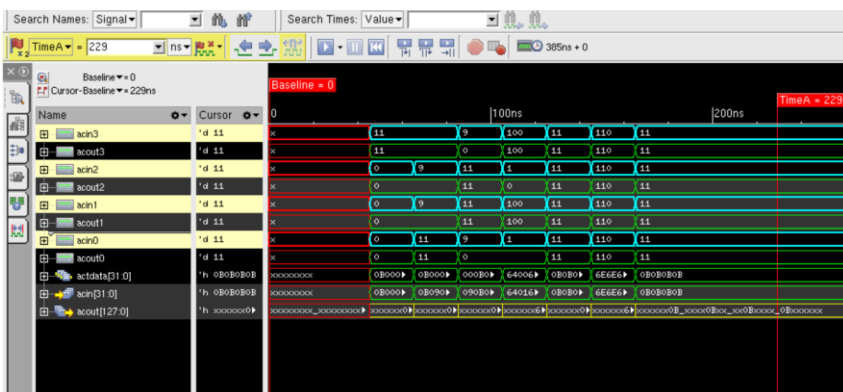


Blue Traces are in inputs while the green traces are outputs

 Question 2: Systolic Array

In this section we are going to define a 4x4 Systolic array using the MAC unit described in question 1. A 4x4 systolic array contains 16 MAC units connected as shown below. The blue lines represent the data from the A matrix. Yellow lines represent the data from the Weight matrix and the Green line represent the Product output of each MAC. As shown below the Weight and Products are connected to the next MAC in the same column while the A data lines are connected to the next MAC in the same row.



The systolic array is first initialized with the weight matrix using 4 cycles and then the A matrix is passed on as shown below. The product output of each MAC in the Last row will contain the required output of the matrix multiplication. The validity of the output product is maintained by a data valid signal that travels parallel to it. The whole process takes about 14 clock cycles. This includes the weight loading, A loading and product output flushing. It is described as shown below:

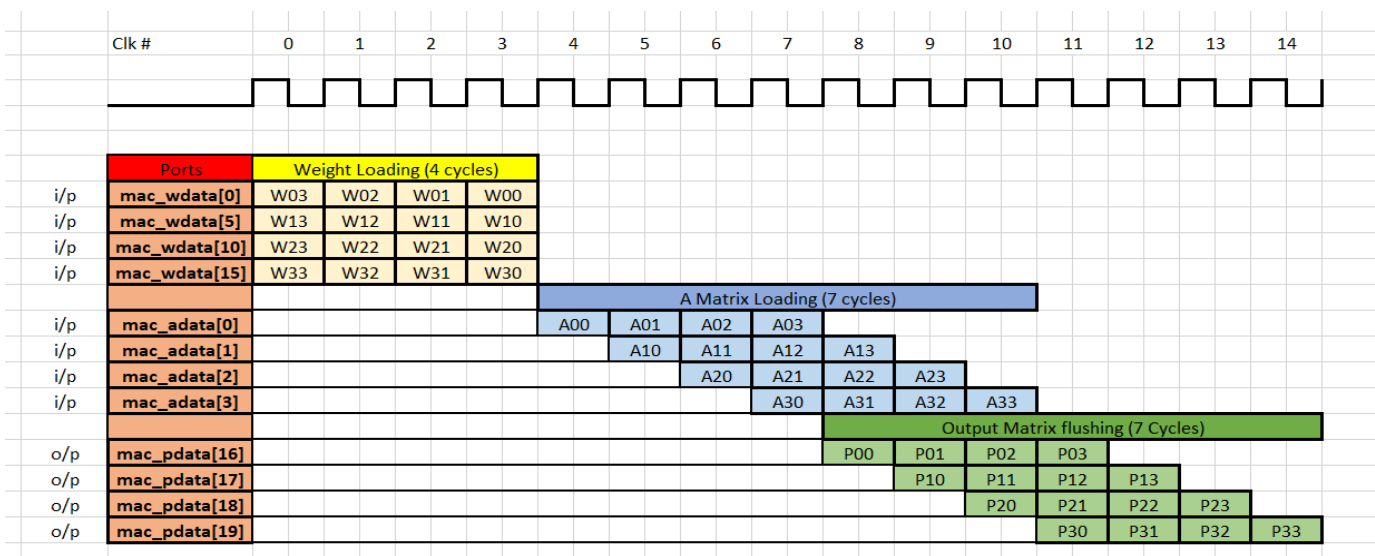

The output of each column would have the below calculations within them:

	Column 1 - Output	Column 2 - Output	Column 3 - Output	Column 4 - Output
Clk #4	$W00*A00 + W01*A10 + W02*A20 + W03*A30$			
Clk #5	$W00*A01 + W01*A11 + W02*A21 + W03*A31$	$W10*A00 + W11*A10 + W12*A20 + W13*A30$		
Clk #6	$W00*A02 + W01*A12 + W02*A22 + W03*A32$	$W10*A01 + W11*A11 + W12*A21 + W13*A31$	$W20*A00 + W21*A10 + W22*A20 + W23*A30$	
Clk #7	$W00*A03 + W01*A13 + W02*A23 + W03*A33$	$W10*A02 + W11*A12 + W12*A22 + W13*A32$	$W20*A01 + W21*A11 + W22*A21 + W23*A31$	$W30*A00 + W31*A10 + W32*A20 + W33*A30$
Clk #8		$W10*A03 + W11*A13 + W12*A23 + W13*A33$	$W20*A02 + W21*A12 + W22*A22 + W23*A32$	$W30*A01 + W31*A11 + W32*A21 + W33*A31$
Clk #9			$W20*A03 + W21*A13 + W22*A23 + W23*A33$	$W30*A02 + W31*A12 + W32*A22 + W33*A32$
Clk #10				$W30*A03 + W31*A13 + W32*A23 + W33*A33$


```

genvar m,j;
generate
  for(m=0;m<4;m=m+1)begin
    for(j=0;j<4;j=j+1)begin
      mac mc(
        .pout(mac_pdata[(j*5)+m+1]),
        .dv_pout(mac_pdv[(j*5)+m+1]),
        .aout(mac_adata[(m*5)+j+1]),
        .dv_aout(mac_adv[(m*5)+j+1]),
        .wout(mac_wdata[(j*5)+m+1]),
        .dv_wout(mac_wdv[(j*5)+m+1]),
        .ain(mac_adata[(m*5)+j]),
        .dv_ain(mac_adv[(m*5)+j]),
        .win(mac_wdata[(j*5)+m]),
        .dv_win(mac_wdv[(j*5)+m]),
        .init_win(init_win),
        .pin(mac_pdata[(j*5)+m]),
        .dv_pin(mac_pdv[(j*5)+m]),
        .dv_mult(dv_mult),
        .clk(clk),
        .rst(rst)
      );
    end
  end
// assign mac_pdata [m*5]= 24'd0;


```

The systolic array is defined by this generate statement. The Connections across the rows (A matrix) are handled by the variable “j” while the connections across the column (weight and product) are handled by the variable “m”.

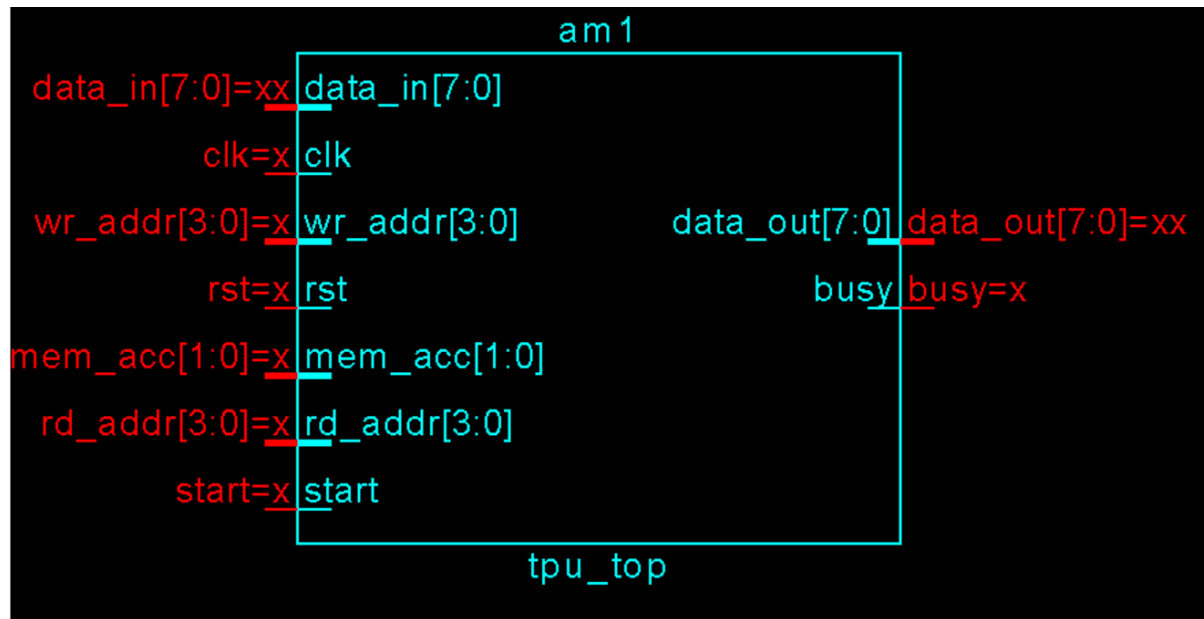Question 3 Testing the TPU using iverilog and cadence



The TPU consists of the systolic array, activation unit and the quantization unit. Additionally there is a 32 Byte RTL memory called feature memory and another 16 byte rtl memory called weight memory. The test bench would load the weight matrix and the A matrix using the data_in bus and the wr_addr bus. The test bench should make sure to use mem_acc = 2'b01 for accessing the A matrix and mem_acc = 2'b10 for accessing the weight matrix. After this the test bench is expected to give a 1'b1 for one clock cycle in the start input port of the tpu_top. This would tell the tpu_top that the 2 matrix's are loaded into the feature and weight memory and to start the multiplication process. When the tpu_top start the weight loading the busy signal will go high. It will only go down one the products are written into the upper 16 bytes of the feature memory. The busy signal going down is an indication to the testbench that the multiplication is complete and output matrix is ready to be read out. The rd_addr and data_out ports are used for this process. Further more the mem_acc = 2'b11 to access the feature memory.

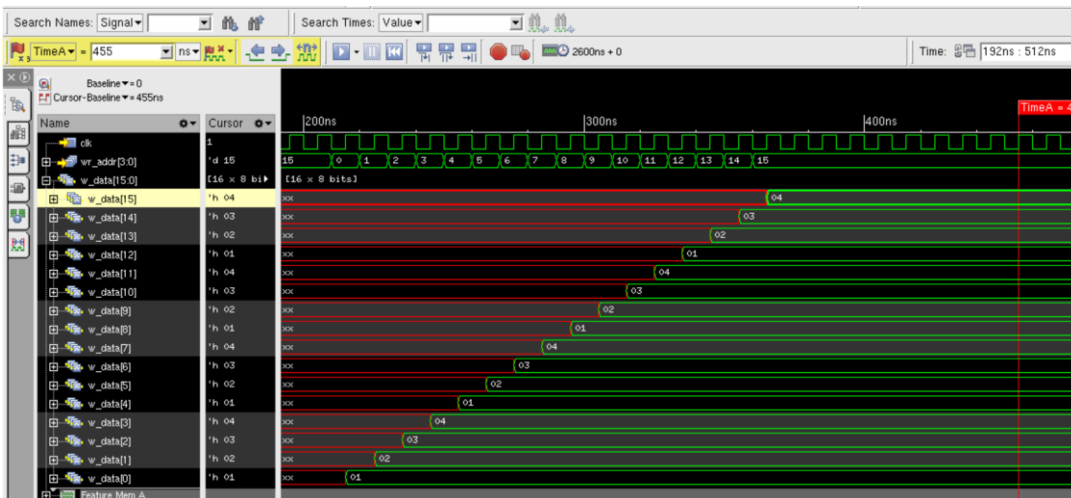

Test Bench Writing A Matrix into the TPU

```


always @(negedge clk) begin
    if(rst)begin
        wr_addr <= 4'd0;
        data_in <= 8'd0;
        mem_acc <= 2'b00;
    end
    else if(start_a)begin
        wr_addr <= count;
        mem_acc <= 2'b01;
        data_in <= a[count];
    end
    else if(start_w)begin
        wr_addr <= count;
        mem_acc <= 2'b10;
        data_in <= w[count];
    end
    else if(start_p)begin
        rd_addr <= count;
        mem_acc <= 2'b11;
        p[count-1] <= data_out;
    end
end

```

```

n=10
start_a = 1'b1;
#20
wait(count == 4'd0)
start_a = 1'b0;

```

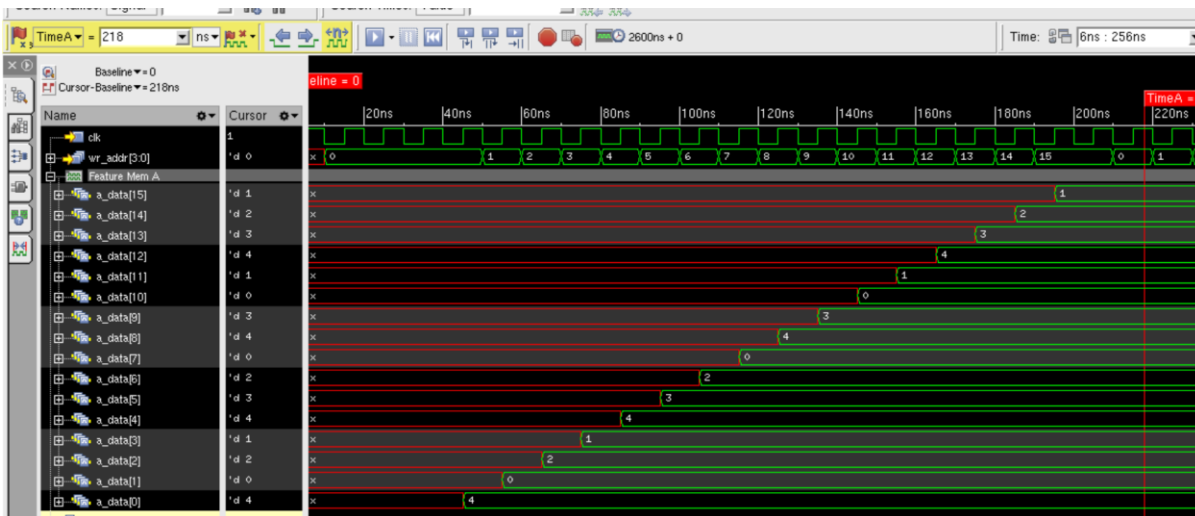


After the Start signal is given the TPU Starts loading the Weight matrix using 4 clock cycles. A counter is used to count upto the 4 cycles required to load the matrix.

```
always @(posedge clk or posedge rst) begin
    if(rst)begin
        init_cnt <= 2'd3;
        init_win <= 1'b0;
    end
    else if(busy && start && (init_cnt == 2'd3))begin
        init_cnt <= init_cnt+1;
        init_win <= 1'b1;
    end
    else if(init_win)begin
        if(init_cnt == 2'd3)
            init_win <= 1'b0;
        else
            init_cnt <= init_cnt+1;
    end
end
end
```

init_cnt is the counter and init_win is the datavalid.
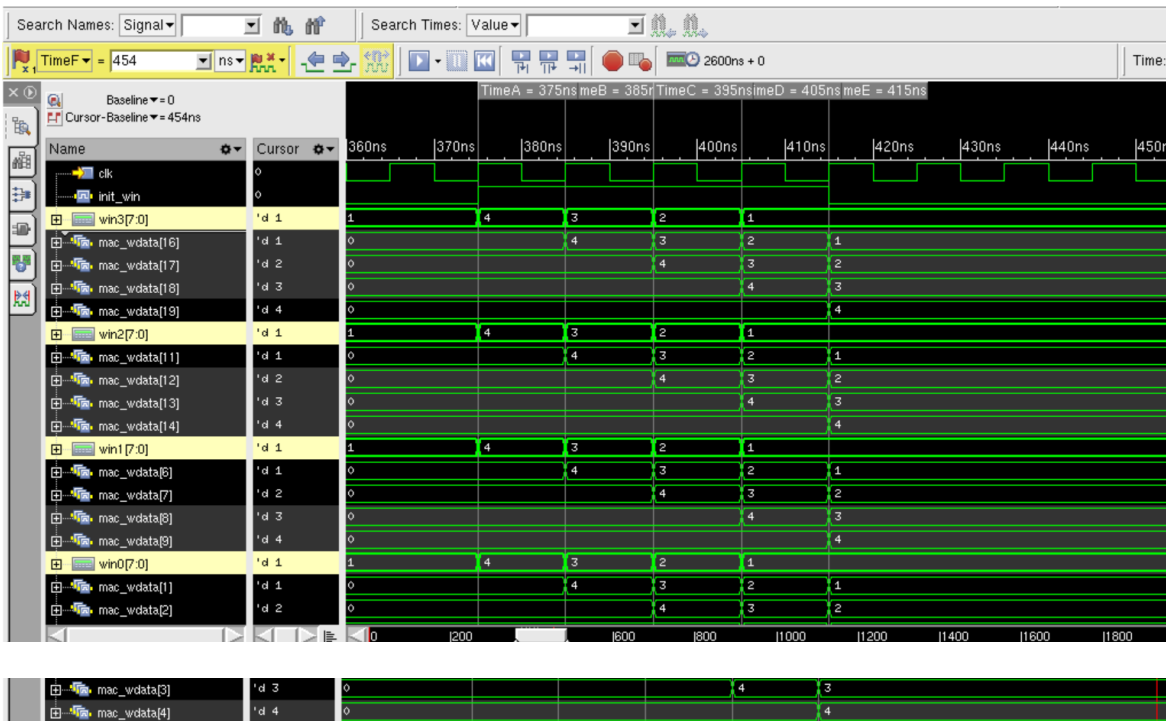
```
assign mac_wdata[m*5] = w_data[(m*4) - init_cnt + 3];
assign mac_wdv[m*5] = init_win;
```



Input weight ports of the systolic array are highlighted. Init_win is on four 4 cycles and the values are flopped dwnwd

After the Init is done, the A matrix is started to load and the multiplication process starts. The A matrix is loaded across 7 cycles and they are counted up by using another counter called mul_cnt. The same counter is used to flush out the output products.

```
reg multiply;
always@(*) begin
    if(rst)
        multiply <= 1'b0;
    else if(busy && mac_wdv[4])
        multiply <= 1'b1;
    else if(mul_cnt == 4'd10)
        multiply <= 1'b0;
    else
        multiply <= multiply;
end


always@(posedge clk or posedge rst)begin
    if(rst)
        mul_cnt <= 4'd0;
    else if(multiply)
        mul_cnt <= mul_cnt +1;
    else
        mul_cnt <= 4'd0;
end
```

```
always @(*)begin
    if(rst)begin
        mac_radv[0] <= 1'b0;
    end
    else if(multiply && (mul_cnt<=3))begin
        mac_radv[0] <= 1'b1;
        mac_ad[0] <= a_data[mul_cnt];
    end
    else
        mac_radv[0] <= 1'b0;
end
```

```
always @(*) begin
    if(rst)begin
        mac_radv[1] <= 1'b0;
    end
    else if(multiply && (mul_cnt>=1)&&(mul_cnt<=4))begin
        mac_radv[1] <= 1'b1;
        mac_ad[1] <= a_data[mul_cnt+4'd3];
    end
    else
        mac_radv[1] <= 1'b0;
end
```

```
always @(*) begin
    if(rst)begin
        mac_radv[2] <= 1'b0;
    end
    else if(multiply && (mul_cnt>=2)&&(mul_cnt<=5))begin
        mac_radv[2] <= 1'b1;
        mac_ad[2] <= a_data[mul_cnt+4'd6];
    end
    else
        mac_radv[2] <= 1'b0;
end
```
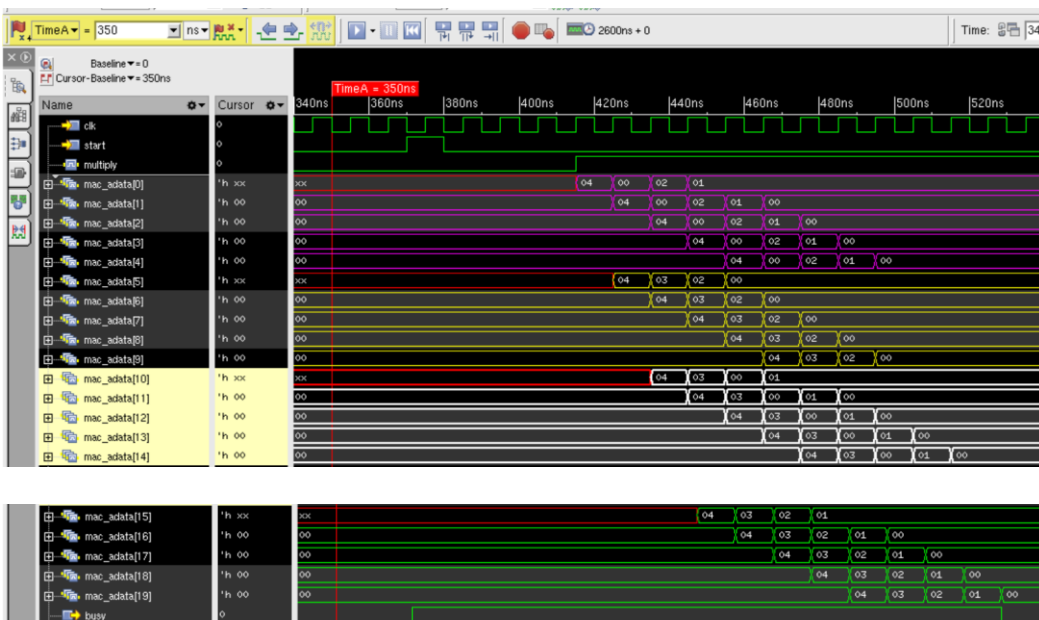
```
always @(*) begin
    if(rst)begin
        mac_radv[3] <= 1'b0;
    end
    else if(multiply && (mul_cnt>=3)&&(mul_cnt<=6))begin
        mac_radv[3] <= 1'b1;
        mac_ad[3] <= a_data[mul_cnt+4'd9];
    end
    else
        mac_radv[3] <= 1'b0;
end
```





mac_adata[0] starts followed by mac_adata[5],mac_adata[10],mac_adata[15]

The values loaded into these port is determined by the mapping provided in question 2.


After 4 cycles of A being loaded, we will get the first Product output in parallel. These products are then routed to the quantization and activation units respectively

	Column 1 - Output	Column 2 - Output	Column 3 - Output	Column 4 - Output
Clk #4	$1*4 + 2*4 + 3*4 + 4*4 = 40$			
Clk #5	$1*0 + 2*3 + 3*3 + 4*3 = 27$	$1*4 + 2*4 + 3*4 + 4*4 = 40$		
Clk #6	$1*2 + 2*2 + 3*0 + 4*2 = 14$	$1*0 + 2*3 + 3*3 + 4*3 = 27$	$1*4 + 2*4 + 3*4 + 4*4 = 40$	
Clk #7	$1*1 + 2*0 + 3*1 + 4*1 = 8$	$1*2 + 2*2 + 3*0 + 4*2 = 14$	$1*0 + 2*3 + 3*3 + 4*3 = 27$	$1*4 + 2*4 + 3*4 + 4*4 = 40$
Clk #8		$1*1 + 2*0 + 3*1 + 4*1 = 8$	$1*2 + 2*2 + 3*0 + 4*2 = 14$	$1*0 + 2*3 + 3*3 + 4*3 = 27$
Clk #9			$1*1 + 2*0 + 3*1 + 4*1 = 8$	$1*2 + 2*2 + 3*0 + 4*2 = 14$
Clk #10				$1*1 + 2*0 + 3*1 + 4*1 = 8$

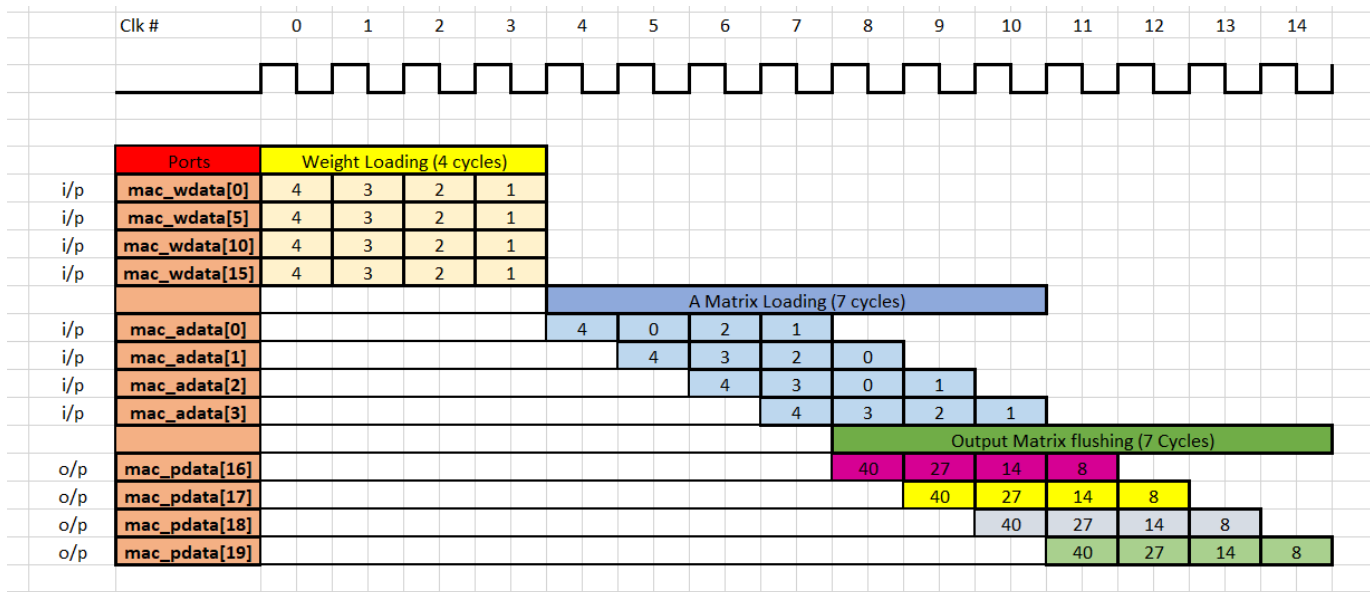

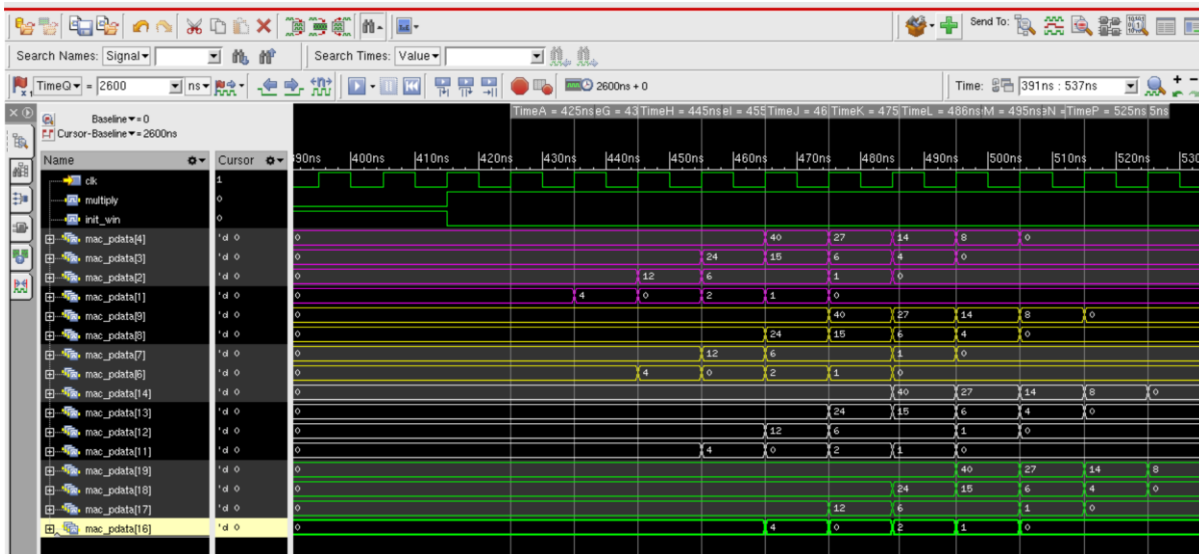

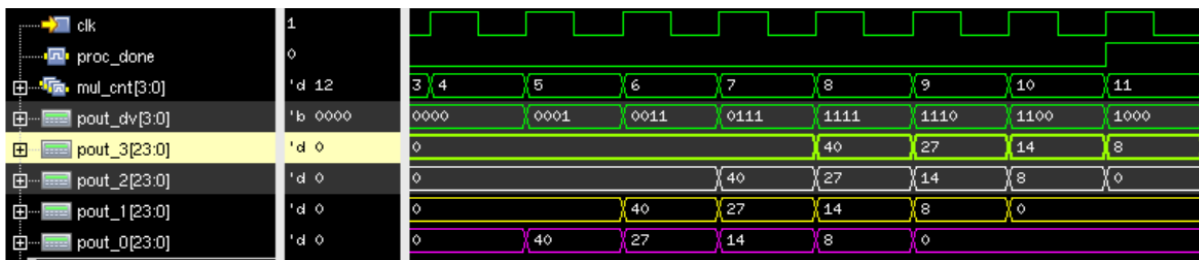Note that the colour coding of the outputs are the same for easy comparison.




Once all the outputs are flushed out, the proc_done signal goes up which indicates to the testbench the output is ready to be read out. After the outputs are flushed, it is taken parallel into the quantization and activation unit of the TPU. The output of which are then stored into the feature memory as shown below

```

activ a1(.acout(act_data),
        .dv_acout(proc_done),
        .acin(quant_dout),
        .dv_acin(quant_dvout),
        .rst(rst)
);


quant q1(.rst(rst),
        .dv_pin(sys_dv),
        .pin(sys_data),
        .qout(quant_dout),
        .dv_qout(quant_dvout)
);

```

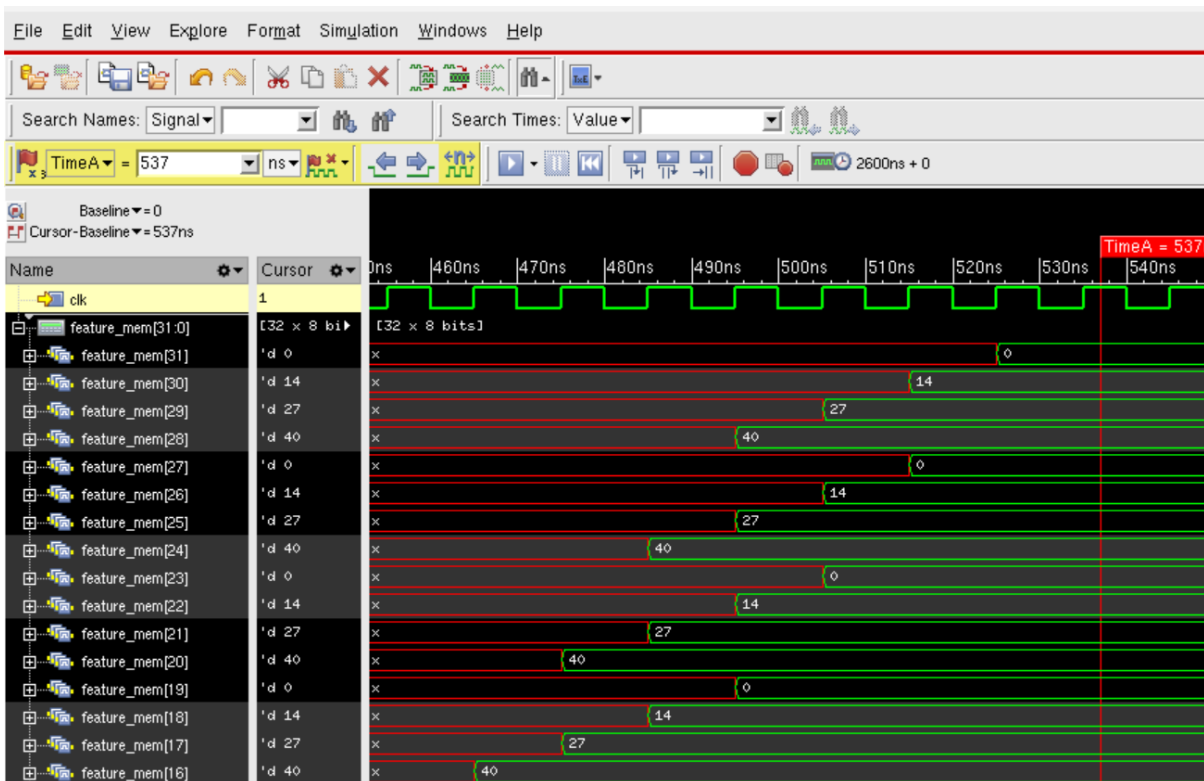

Note that the output value of 8 has now become 0 due to the activation unit. ($8 < 10$).

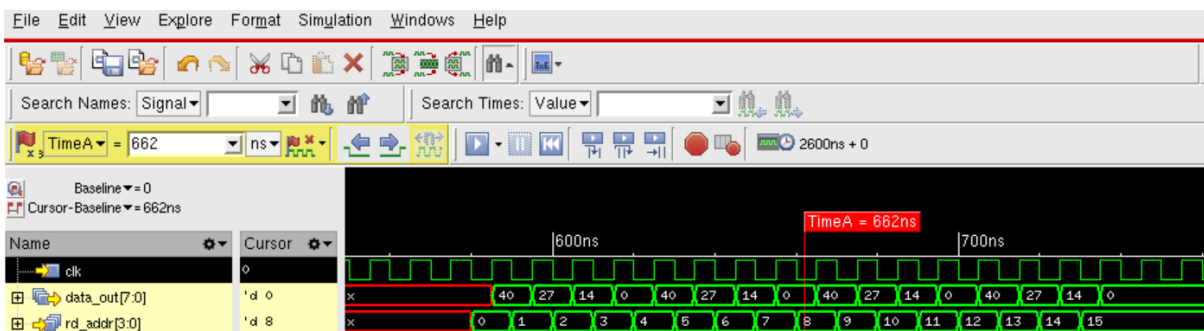The testbench after detecting the busy signal has gone down, then readsout the feature memory for display.



```
skanda@LAPTOP-3RMLJVKC:~/asic_design/midterm$ iverilog tb_tpu_top.v tpu_top.v quant.v mac.v activ.v
skanda@LAPTOP-3RMLJVKC:~/asic_design/midterm$ vvp a.out

W_matrix = 1 2 3 4
            1 2 3 4
            1 2 3 4
            1 2 3 4

A_Matrix = 4 0 2 1
            4 3 2 0
            4 3 0 1
            4 3 2 1

P_Matrix = 40 27 14 0
            40 27 14 0
            40 27 14 0
            40 27 14 0

VCD info: dumpfile wave_tpu_top.vcd opened for output.
```



```

-bash-4.2$ /network/rit/lab/ceashpc/software/cadence/XCELIUM1909/tools.lnx86/bin/64bit/xrun -gui -access rwc /network/rit/home
/sb914816/final_midterm/tb_tpu_top.v tpu_top.v mac.v quant.v activ.v
TOOL:  xrun(64)      19.09-s001: Started on Mar 19, 2024 at 19:58:54 EDT
xrun(64): 19.09-s001: (c) Copyright 1995-2019 Cadence Design Systems, Inc.
Recompiling... reason: checksum check failure for module worklib.stimulus:v (VST).
file: /network/rit/home/sb914816/final_midterm/tb_tpu_top.v
  module worklib.stimulus:v
    errors: 0, warnings: 0
    Caching library 'worklib' ..... Done
  Elaborating the design hierarchy:
  Top level design units:
    stimulus
  Building instance overlay tables: ..... Done
  Generating native compiled code:
    worklib.stimulus:v <0x75cfcc2e>
      streams: 21, words: 26664
    worklib.tpu_top:v <0x043738af>
      streams: 113, words: 32382
  Building instance specific data structures.
  Loading native compiled code: ..... Done
  Design hierarchy summary:
      Instances  Unique
  Modules:      20      5
  Registers:    180     45
  Scalar wires: 102     -
  Expanded wires: 96     4
  Vectored wires: 84     -
  Always blocks: 136    25
  Initial blocks: 4      4
  Cont. assignments: 41   15
  Pseudo assignments: 39  15
  Writing initial simulation snapshot: worklib.stimulus:v

```